Nume student: Danciu Camelia-Maria

Grupa 2133

Project SCIA

1. Tematica proiectului

Specificatii generale:

ETAJ 1:

Sursa semnal:4(current differential)

Amplitudine minima(pt castig maxim PGA):2.00e-05

Amplitudine maxima(pt castig minim PGA):5.02e-05

Unitate masura(A diferential)

Tip etaj1:6(AI cu 2AO;Inversor,intrare I)

|Castig| etaj 1(liniar):10K

ETAJ 2:

Tip etaj 2:9(Trece banda; 1 AO V-V, Delyiannis)

|H0|castig liniar in banda de trecere:1

Rintrare minim: $2k\Omega$

Banda:5khz

Q = 1.41

ETAJ 3:

Tip etaj 3:5(RF serie)

Castig minim[dB]:2

Rezolutie(pas minim[dB]):2

Nr. pasi:5

Castig maxim[dB]:20

Rintrare minim:-

ETAJ 4:


Tip etaj:6(redresor dubla alternanta FWR v6)

Castig(liniar):2

TIP AO:4(LT6234;+/-5V)

2. Dimensionarea etajului 1 / 2 / 3 / 4

ETAJUL 1:

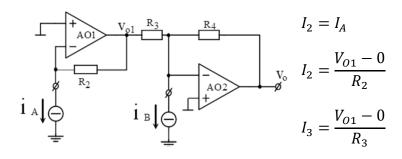

$$\Rightarrow$$
 Daca $R_3 = R_2$, $I_2 = I_3 = I_A$


$$I_3 + I_4 = I_B => I_4 = I_B - I_3$$
 , $I_3 = I_A => V_{OUT} = R_4 * (I_B - I_A)$

$$A_V = \frac{v_{OUT}}{v_{IN}} = R_4 \text{ (castigul)} => R_4 = 10k\Omega$$
 Aleg $R_2 = R_3 = 10k\Omega$ Aleg $I_A = 0.5A$ $I_B = -0.5A$

Amplitudine maxima(pt castig PGA maxim):5,02*e-05(A diferential) Amplitudine minima(pt castig PGA minim):2*e-05(A diferential)

$$\Rightarrow$$
 Offset= $(5,02*e-05+2*e-05)/2=3.51*e-05=35.1uA$

ETAJUL 2:

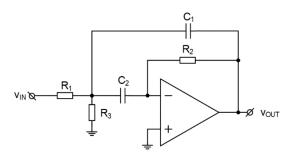

Parametrii functiei de transfer:

$$H_0 = \frac{R_2}{R_1} \cdot \frac{C_2}{C_1 + C_2};$$

$$\omega_0 = \sqrt{\frac{R_1 + R_3}{R_1 R_2 R_3 C_1 C_2}};$$

$$Q = \sqrt{R_2 \frac{R_1 + R_3}{R_1 R_3}} \cdot \frac{\sqrt{C_1 C_2}}{C_1 + C_2}.$$

Aleg:

$$R = R_1 \parallel R_3;$$

$$R_2 = r \cdot R;$$

$$C_1 = C;$$

$$C_2 = \frac{C}{k};$$

$$H_0 = \frac{r \cdot R}{k} \cdot \frac{1}{k} \cdot \rho_0 = \frac{1}{k}$$

$$\begin{split} H_0 &= \frac{r \cdot R}{R_1} \cdot \frac{1}{k+1}; \omega_0 = \frac{1}{R \cdot C} \cdot \sqrt{\frac{k}{r}}; \mathcal{Q} = \frac{\sqrt{r} \cdot \sqrt{k}}{k+1}. \\ &a = \mathcal{Q} \cdot \omega_0 \cdot R \cdot C; \\ k &= \frac{a}{1-a}; r = \frac{k}{\omega_0^2 \cdot R^2 \cdot C^2}; R_1 = \frac{r \cdot R}{H_0} \cdot \frac{1}{k+1}; R_2 = r \cdot R; R_3 = \frac{R_1 \cdot R}{R_1 - R} \end{split}$$

 $|H_0| = 1$ (castig liniar in banda de trecere)

$$R_{in_{minim}} = 2k,$$

$$B_{-3dB} = 5khz$$

$$B_{-3dB} = 5kh$$

$$Q=1.41$$

$$R=20k\Omega$$

$$R_2 = r * R = 16 * 20 = 320k\Omega$$

$$f_0 = 5khz$$

$$2 * \pi * 5 * 10^{3} = \frac{1}{RC} * \sqrt{\frac{k}{r}} = > \pi * 10^{4} = \frac{1}{20k * C} * \sqrt{\frac{0.16}{16}} = \frac{0.1}{20k * C} = >$$

$$C = \frac{1}{20k * \pi * 10^{4} * 10} = 10^{-9} * \frac{1}{2 * \pi} \approx 0.16nF$$

$$C_1 = C = 0.16nF$$


$$C_2 = \frac{C}{k} = \frac{0.16nF}{0.16} = 1nF$$

$$H_0 = \frac{R_2}{R_1} * \frac{1}{1+k}$$

$$R_1 = \frac{R_2}{k+1} = \frac{320k}{1.16} = 275.86 \text{k}\Omega$$

$$R_3 = \frac{R_1 * R}{R_1 - R} = \frac{275.86k * 20k}{255.86k} = 21.56k\Omega$$

ETAJUL 3:

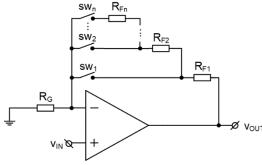

$$R_{F1} = (4-1)*R_G = 3*100\Omega = 300\Omega$$

Sw2=on:
$$A_V = 5$$

$$R_{ech} = R_{F1} + R_{F2}$$

$$R_{F1} + R_{F2} = (5-1)R_G = 4R_G$$

$$R_{F2} = 4R_G - R_{F1} =$$

$$= 400 - 300 =$$

 $= 100\Omega$

Sw3=on: $A_V = 6.3$

$$R_{ech} = R_{F1} + R_{F2} + R_{F3}$$

$$R_{F1} + R_{F2} + R_{F3} = 5.3R_G$$

$$R_{F3} = 5R_G - R_{F2} - R_{F1} =$$

 $=130\Omega$

Sw4=on: $A_V = 8$

$$R_{ech} = R_{F1} + R_{F2} + R_{F3} + R_{F4}$$

$$R_{F1} + R_{F2} + R_{F3} + R_{F4} = 7R_G$$

$$R_{F4} = 8R_G - R_{F1} - R_{F2} - R_{F3} - R_{F4} =$$

 $=170\Omega$

$$\begin{split} A_{dB} &= \{12dB; 14dB; 16dB; 18dB; 18dB; 20dB\}, \\ A_{V} &= 10^{\frac{A_{dB}}{20}} \Longrightarrow |A_{V}| = \{4\frac{v}{v}; 5\frac{v}{v}; 6.3\frac{v}{v}; 8\frac{v}{v}; 10\frac{v}{v}\} \end{split}$$

AO neinversor=>
$$A_V$$
= $(1+\frac{R_{ech}}{R_G})$

Sw1=on(castig minim): $A_V = 4$

$$R_{ech} = R_{F1}, A_V = (1 + \frac{R_{ech}}{R_G}) = > R_{F1} = (A_V - 1)R_G$$


Aleg $R_G = 100\Omega$

Sw5=on:
$$A_V = 10$$

$$\begin{split} R_{ech} &= R_{F1} + R_{F2} + R_{F3} + R_{F4} + R_{F5} \\ R_{F1} &+ R_{F2} + R_{F3} + R_{F4} + R_{F5} = 9R_G \\ R_{F5} &= 9R_G - R_{F1} - R_{F2} - R_{F3} - R_{F4} = \\ &= 900 \text{-} 300 \text{-} 100 \text{-} 130 \text{-} 170 = \end{split}$$

 $=200\Omega$

ETAJUL 4:

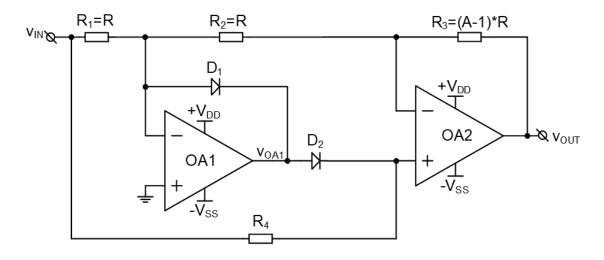

Presupunem D1,D2=OFF


$$I) V_{IN} = -V_{SS}$$

Pentru AO1:

$$\begin{split} V^{+} &= 0 \\ V^{-} &= -V_{SS} \rbrace => V_{OA1} \nearrow V_{DD} \\ V_{OA} &= a_{\infty} (V^{+} - V^{-}) = \infty (0 + V_{SS}) > 0 => V_{OA1} \nearrow V_{DD} \end{split}$$

$$V_{AK1} = -V_{SS} - V_{DD} < 0 => D1 = OFF$$
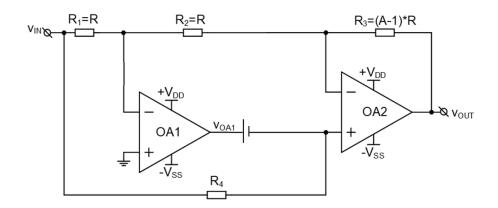
$$V_{AK2} = V_{DD} - (-V_{SS}) > 0 => D2 = ON$$



OA1 in bucla de reactie negative deoarece ${V_2}^+ = {V_2}^- \quad => \ {V_1}^+ = {V_1}^- = 0$

$$=> I_{R1} = \frac{V_{IN}}{R_1}$$

$$I_{R1} = I_{R2} = I_{R3} = \frac{V_{IN}}{R_1}$$

$$V_{OUT} = 0 - I_{R1}(R_2 + R_3)$$

$$V_{OUT} = -\frac{V_{IN}}{R_1}(R_2 + R_3) = -(\frac{R_2 + R_3}{R_1})V_{IN}$$

II)
$$V_{IN} = V_{DD}$$


Pentru AO1:

$$\begin{array}{l} V^{+} = 0 \\ V^{-} = V_{DD} \end{array} \} => \ V_{OA1} \searrow - V_{SS} \\ \end{array}$$

$$V_{OA} = a_{\infty}(V^+ - V^-) = \infty(0 - V_{DD}) < 0 = > V_{OA1} \setminus -V_{SS}$$

$$V_{AK1} = V_{DD} - (-V_{SS}) > 0 => D1 = ON$$
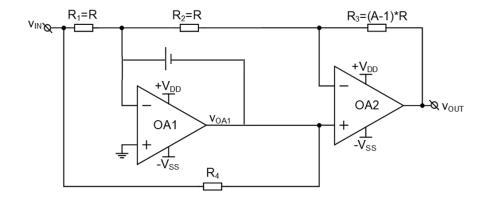
$$V_{AK2} = -V_{SS} - V_{DD} < 0 \implies D2 = OFF$$



Exista Reactie Negativa prin D1:

$$V_1^+ = V_1^- \implies$$
 AO2 neinversor

$$V_{OUT} = (1 + \frac{R_3}{R_2})V_{IN}$$

CONDITIA REDRESOR BIALTERNANTA: $R_1 = R_2$

Concluzie:

$$V_{OUT} = \begin{cases} -\frac{R_3 + R_2}{R_1} V_{IN}, V_{IN} < 0 \\ 1 + \frac{R_3}{R_2} V_{IN}, \quad V_{IN} > 0 \end{cases} \Leftrightarrow V_{OUT} = \begin{cases} -A * V_{IN}, V_{IN} < 0 \\ A * V_{IN}, \quad V_{IN} > 0 \end{cases}$$

$$R_1 = R_2 \implies A=1 + \frac{R_3}{R_2}$$

 $|H_0|=2(liniar)$

Aleg
$$R_1 = R_3 = R_3 = R_4 = 10 \text{k}\Omega$$

1. Caracterizarea etajului 1 / 2 / 3 / 4. Verificarea si caracterizarea interfetei analogice

Etajul 1:

```
Parametrii DCOP:
Starting Gmin stepping
Gmin = 10
Gmin = 1.07374
Gmin = 0.115292
Gmin = 0.0123794
Gmin = 0.00132923
Gmin = 0.000142725
Gmin = 1.5325e-05
Gmin = 1.6455e-06
Gmin = 1.76685e-07
Gmin = 1.89714e-08
vernier = 0.5
vernier = 0.25
vernier = 0.125
Gmin = 1.49241e-08
vernier = 0.166667
vernier = 0.222222
Gmin = 1.00912e-08
vernier = 0.296296
Gmin = 5.38725e-09
vernier = 0.395061
vernier = 0.526748
Gmin = 1.96664e-09
vernier = 0.702331
vernier = 0.936441
Gmin = 4.16555e-10
vernier = 1
Gmin = 4.76818e-11
Gmin = 5.11979e-12
Gmin = 5.49733e-13
Gmin = 0
Gmin stepping succeeded in finding the operating point.
N-Period=1
Fourier components of V(out)
DC component:0.350998
Harmonic
             Frequency
                                  Fourier
                                                     Normalized
              Phase
                                 Normalized
 Number
                [Hz]
                                 Component
                                                      Component
              [degree]
                                 Phase [deg]
              1.000e+3
                                  1.510e-1
                                                      1.000e+0
    1
```

90.00°

16.92°

2.000e+3

0.00°

1.218e-8

1.839e-9

-73.08°

3	3.000e+3	1.934e-9	1.281e-8
	24.55°	-65.46°	
4	4.000e+3	2.062e-9	1.366e-8
	31.27°	-58.73°	
5	5.000e+3	2.216e-9	1.468e-8
	37.12°	-52.88°	
6	6.000e+3	2.391e-9	1.584e-8
	42.15°	-47.86°	
7	7.000e+3	2.582e-9	1.711e-8
	46.44°	-43.57°	
8	8.000e+3	2.786e-9	1.845e-8
	50.10°	-39.91°	
9	9.000e+3	2.999e-9	1.987e-8
	53.22°	-36.78°	
10	1.000e+4	3.221e-9	2.134e-8
	55.91°	-34.09°	

Partial Harmonic Distortion: 0.000005% Total Harmonic Distortion: 0.000000%

Date: Wed Jan 17 21:40:28 2024 Total elapsed time: 0.233 seconds.

tnom = 27temp = 27

method = modified trap

totiter = 2984 traniter = 2120 tranpoints = 1061 accept = 1058 rejected = 3


matrix size = 25
fillins = 31

solver = Normal


Avg thread counts: 2.9/4.8/4.8/2.9

Matrix Compiler1: 2.90 KB object code size 2.6/1.6/[1.0] Matrix Compiler2: 3.01 KB object code size 0.6/0.7/[0.3]


- Parametrii semnal mic:

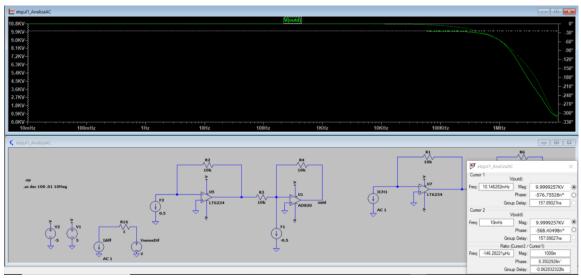

Castig:10kV(liniar)

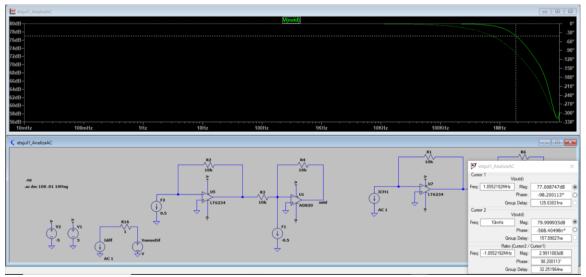


Banda la -3dB:1.85Mhz

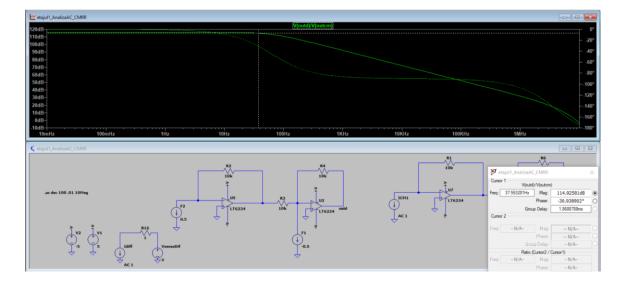

CMRR(factorul de rejectie al modului comun):114.92dB

- Parametrii semnal mare:

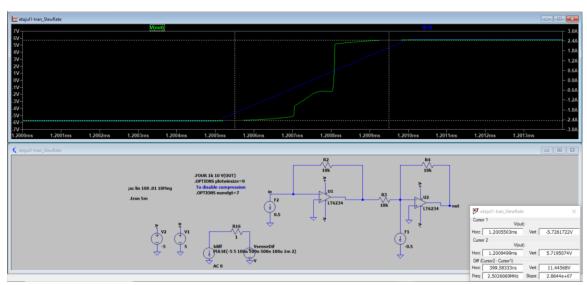

SR:28.64V/us

Etajul 2:

Parametrii DCOP: - Circuit: * C:\Users\danci\OneDrive\Desktop\Proiect SCIA\etajul2\etajul 2.asc - Direct Newton iteration failed to find .op point. (Use ".option noopiter" to skip.) Starting Gmin stepping Gmin = 10Gmin = 1.07374Gmin = 0.115292Gmin = 0.0123794- Gmin = 0.00132923- Gmin = 0.000142725Gmin = 1.5325e-05- Gmin = 1.6455e-06Gmin = 1.76685e-07Gmin = 1.89714e-08vernier = 0.5- vernier = 0.25vernier = 0.125- Gmin = 1.49241e-08vernier = 0.166667 vernier = 0.222222- Gmin = 1.00912e-08- vernier = 0.296296Gmin = 5.38725e-09- vernier = 0.395061vernier = 0.526748Gmin = 1.96664e-09- vernier = 0.702331vernier = 0.936441Gmin = 4.16555e-10- vernier = 1 Gmin = 4.76818e-11Gmin = 5.11979e-12- Gmin = 5.49733e-13Gmin = 0Gmin stepping succeeded in finding the operating point. N-Period=1 Fourier components of V(out_tb) DC component: 0.480015

_				
-	Harmonic	Frequency	Fourier	Normalized
		Phase	Normalized	
-	Number	[Hz]	Component	Component
		[degree]	Phase [deg]	
-	1	1.000e+3	1.501e-1	1.000e+0
		-171.35°	0.00°	

```
2
              2.000e+3
                                  2.371e-7
                                                     1.579e-6
               178.46°
                                   349.81°
              3.000e+3
    3
                                  2.361e-7
                                                     1.573e-6
               177.69°
                                   349.04°
    4
              4.000e+3
                                  2.346e-7
                                                     1.563e-6
               176.92°
                                   348.27°
    5
              5.000e+3
                                  2.328e-7
                                                     1.550e-6
               176.14°
                                   347.49°
    6
              6.000e+3
                                  2.305e-7
                                                     1.535e-6
               175.36°
                                   346.71°
    7
              7.000e+3
                                  2.278e-7
                                                     1.517e-6
               174.57°
                                   345.92°
                                  2.247e-7
              8.000e+3
                                                     1.496e-6
    8
               173.78°
                                   345.13°
    9
              9.000e+3
                                  2.211e-7
                                                     1.473e-6
               172.98°
                                   344.32°
   10
              1.000e+4
                                  2.172e-7
                                                     1.447e-6
               172.16°
                                   343.51°
Partial Harmonic Distortion: 0.000458%
Total Harmonic Distortion:
                             0.006198%
```

Date: Wed Jan 17 22:31:34 2024 Total elapsed time: 0.273 seconds.

tnom = 27temp = 27

method = modified trap

totiter = 2942traniter = 2092

tranpoints = 1047

accept = 1046

rejected = 1

matrix size = 16


fillins = 11

solver = Normal

- Avg thread counts: 2.9/4.8/4.8/2.9

Matrix Compiler1: 1.21 KB object code size 1.4/0.7/[0.7] Matrix Compiler2: 1.66 KB object code size 0.5/0.6/[0.3]

Parametrii semnal mic:

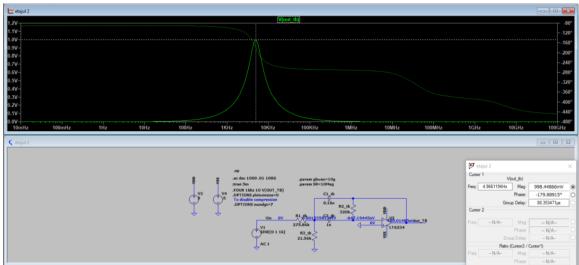

|H0|(Castig liniar in banda de trecere):1 Banda:5kHz

```
10 1.000e+4 2.1726
Partial Harmonic Distortion: 0.0004588
Total Harmonic Distortion: 0.0061988

(THD<1%)
```

ETAJUL 3:

- Parametrii DCOP (pentru primul switch=on; castig minim)
- Circuit: *
 C:\Users\danci\OneDrive\Desktop\Proiect_SCIA\etajul3\etajul 3.asc
- Direct Newton iteration failed to find .op point. (Use ".option noopiter" to skip.)
- Starting Gmin stepping
- Gmin = 10
- Gmin = 1.07374
- Gmin = 0.115292
- Gmin = 0.0123794
- Gmin = 0.00132923
- Gmin = 0.000142725
- Gmin = 1.5325e-05
- Gmin = 1.6455e-06
- Gmin = 1.76685e-07
- Gmin = 1.89714e-08
- Gmin = 2.03704e-09
- Gmin = 2.18725e-10

```
Gmin = 2.34854e-11
Gmin = 2.52173e-12
Gmin = 2.70769e-13
Gmin = 0
Gmin stepping succeeded in finding the operating point.
N-Period=1
Fourier components of V(out)
DC component: 0.00045156
Harmonic
              Frequency
                                   Fourier
                                                      Normalized
               Phase
                                  Normalized
 Number
                [Hz]
                                  Component
                                                       Component
              [degree]
                                  Phase [deg]
    1
               1.000e+3
                                   8.001e-1
                                                       1.000e+0
                 90.00°
                                      0.00°
               2.000e+3
                                   2.638e-6
                                                       3.297e-6
    2
               179.70°
                                     89.70°
    3
               3.000e+3
                                   3.961e-7
                                                       4.951e-7
                 97.39°
                                      7.39°
               4.000e+3
                                   1.296e-7
                                                       1.620e-7
    4
               167.54°
                                     77.55°
    5
               5.000e+3
                                   1.340e-7
                                                       1.675e-7
                177.22°
                                     87.22°
    6
               6.000e+3
                                   1.292e-7
                                                       1.615e-7
               161.32°
                                     71.32°
    7
               7.000e+3
                                   1.285e-7
                                                       1.607e-7
                156.89°
                                     66.89°
    8
               8.000e+3
                                   1.279e-7
                                                       1.598e-7
               154.83°
                                     64.83°
    9
               9.000e+3
                                   1.271e-7
                                                       1.588e-7
                151.65°
                                     61.65°
   10
               1.000e+4
                                   1.263e-7
                                                       1.578e-7
```

58.13°

148.13° Partial Harmonic Distortion: 0.000336% 0.013323% Total Harmonic Distortion:

Date: Wed Jan 17 22:55:54 2024 Total elapsed time: 0.503 seconds.

tnom = 27temp = 27

method = modified trap

totiter = 2608traniter = 2116

tranpoints = 1059

accept = 1055

rejected = 4

matrix size = 60

fillins = 45

solver = Normal

- Avg thread counts: 2.9/4.8/4.8/2.9
- Matrix Compiler1: 5.67 KB object code size 3.3/1.8/[1.0]
- Matrix Compiler2: 6.42 KB object code size 1.6/1.7/[0.9]
- Parametrii DCOP (pentru ultimul switch=on; castig maxim)
- Circuit: *

C:\Users\danci\OneDrive\Desktop\Proiect_SCIA\etajul3\etajul 3.asc

_


- Direct Newton iteration failed to find .op point. (Use ".option noopiter" to skip.)
- Starting Gmin stepping
- Gmin = 10
- Gmin = 1.07374
- Gmin = 0.115292
- Gmin = 0.0123794
- Gmin = 0.00132923
- Gmin = 0.000142725
- Gmin = 1.5325e-05
- Gmin = 1.6455e-06
- Gmin = 1.76685e-07
- Gmin = 1.89714e-08
- Gmin = 2.03704e-09
- Gmin = 2.18725e-10
- Gmin = 2.34854e-11
- Gmin = 2.52173e-12
- Gmin = 2.70769e-13
- Gmin = 0
- Gmin stepping succeeded in finding the operating point.
- N-Period=1
- Fourier components of V(out)
- DC component:0.00134897

-	Harmonic	Frequency	Fourier					
		Phase	Normalized					
-	Number	[Hz]	Component	Component				
		[degree]	Phase [deg]					
-	1	1.000e+3	1.999e+0	1.000e+0				
		90.00°	0.00°					
-	2	2.000e+3	2.536e-6	1.269e-6				
		179.45°	89.45°					
-	3	3.000e+3	1.056e-6	5.286e-7				
		81.09°	-8.92°					
-	4	4.000e+3	5.972e-8	2.988e-8				
		121.61°	31.60°					
-	5	5.000e+3	5.407e-8	2.705e-8				
		-172.42°	-262.42°					
-	6	6.000e+3	8.227e-8	4.117e-8				
		112.75°	22.75°					
-	7	7.000e+3	9.912e-8	4.960e-8				
		107.20°	17.20°					


```
8
               8.000e+3
                                  1.060e-7
                                                      5.302e-8
               107.71°
                                    17.71°
    9
               9.000e+3
                                  1.174e-7
                                                      5.874e-8
               106.22°
                                    16.22°
   10
               1.000e+4
                                  1.299e-7
                                                      6.499e-8
               104.55°
                                    14.55°
Partial Harmonic Distortion: 0.000138%
Total Harmonic Distortion:
                              0.011595%
Date: Wed Jan 17 22:57:40 2024
Total elapsed time: 0.388 seconds.
tnom = 27
temp = 27
method = modified trap
totiter = 2631
traniter = 2148
tranpoints = 1075
accept = 1065
rejected = 10
matrix size = 60
fillins = 45
solver = Normal
Avg thread counts: 2.9/4.7/4.7/2.9
Matrix Compiler1: 5.67 KB object code size 2.9/1.5/[1.0]
Matrix Compiler2: 6.42 KB object code size 1.5/1.5/[0.9]
```

Parametrii semnal mic:


Castig minim(12dB):

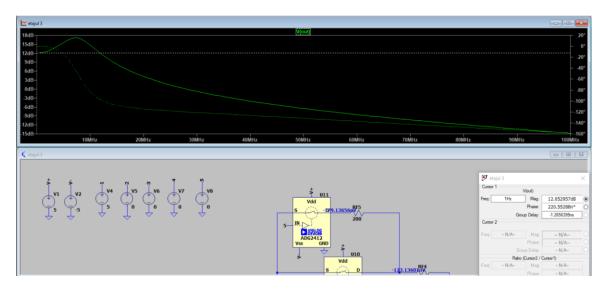


Banda la -3dB:14.33MHz:

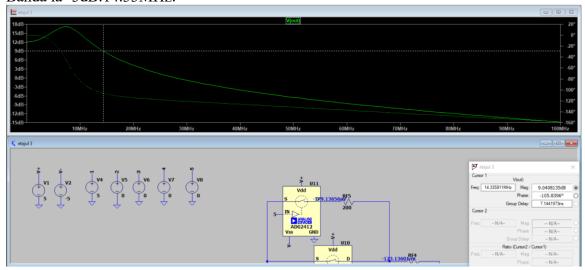


Castig 14dB si banda la -3dB=12.29MHz:

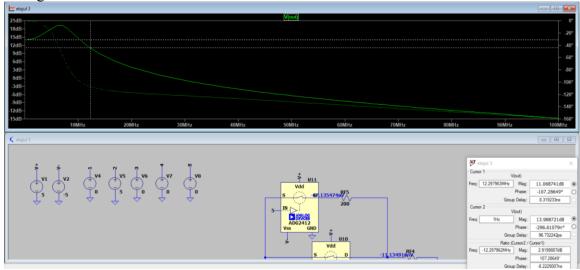


Castig 16dB si banda la -3dB=10.61MHz:

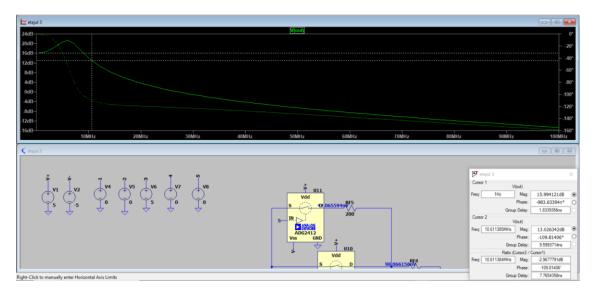

Castig 18dB si banda la -3dB=9.065MHz:

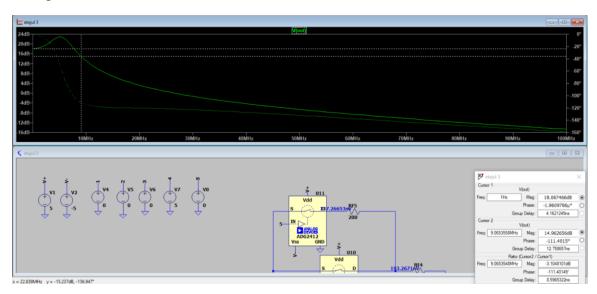

Castig 20dB si banda la -3dB=7.65MHz:

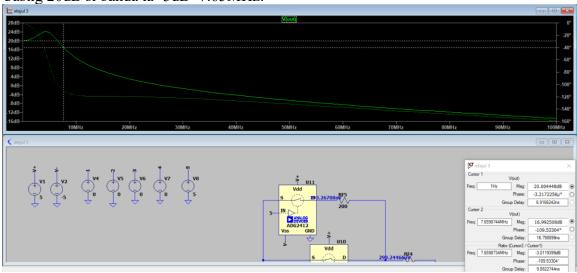

Etajul 4:

Parametrii DCOP:

```
Direct Newton iteration failed to find .op point. (Use ".option noopiter" to skip.)
Starting Gmin stepping
Gmin = 10
Gmin = 1.07374
Gmin = 0.115292
Gmin = 0.0123794
Gmin = 0.00132923
Gmin = 0.000142725
Gmin = 1.5325e-05
Gmin = 1.6455e-06
Gmin = 1.76685e-07
Gmin = 1.89714e-08
vernier = 0.5
```

Circuit: * C:\Users\danci\OneDrive\Desktop\Proiect SCIA\etajul4\etajul

vernier = 0.125
vernier = 0.0625
vernier = 0.03125
vernier = 0.015625
vernier = 0.0078125
vernier = 0.00390625
vernier = 0.00195312
Gmin = 1.89714e-08
vernier = 0.000976562
vernier = 0.000488281
Gmin = 0

Gmin stepping failed

vernier = 0.25

Starting source stepping with srcstepmethod=0

Source Step = 3.0303% Source Step = 24.4318% vernier = 0.015625 Source Step = 24.2661%

Starting source stepping with srcstepmethod=1

Source Step = 3.0303% Source Step = 33.3333% Source Step = 63.6364% Source Step = 93.9394% Source Step = 100% Source Step = 99.1894% Source Step = 99.6629% Source Step = 99.9973% Source Step = 100% Source Step = 100%

Pseudo Transient succeeded in finding the operating point at 325.549 ms.

N-Period=1

Fourier components of V(out) DC component: 0.0180656

Harmonic	Frequency	Fourier	Normalized
	Phase	Normalized	
Number	[Hz]	Component	Component
	[degree]	Phase [deg]	
1	1.000e+3	1.994e+0	1.000e+0
	-89.96°	0.00°	
2	2.000e+3	5.724e-3	2.871e-3
	-179.91°	-89.95°	
3	3.000e+3	5.250e-3	2.633e-3
	-89.87°	0.10°	
4	4.000e+3	4.646e-3	2.330e-3
	0.18°	90.14°	
5	5.000e+3	3.962e-3	1.987e-3
	90.22°	180.18°	
6	6.000e+3	3.249e-3	1.629e-3
	-179.73°	-89.77°	
7	7.000e+3	2.554e-3	1.281e-3
	-89.69°	0.27°	
8	8.000e+3	1.917e-3	9.614e-4
	0.35°	90.31°	
9	9.000e+3	1.363e-3	6.838e-4
	90.39°	180.36°	
10	1.000e+4	9.087e-4	4.558e-4
	-179.56°	-89.60°	

Partial Harmonic Distortion: 0.551785% Total Harmonic Distortion: 0.552760%


Date: Thu Jan 18 00:06:08 2024 Total elapsed time: 0.951 seconds.

temp = 27
method = modified trap
totiter = 14970
traniter = 2254
tranpoints = 1128
accept = 1103
rejected = 35
matrix size = 24
fillins = 62
solver = Normal


Avg thread counts: 2.8/4.6/4.6/2.8

Matrix Compiler1: 4.77 KB object code size 1.2/0.6/[0.6] Matrix Compiler2: 3.68 KB object code size 1.0/1.0/[0.5]


Castigul liniar:2

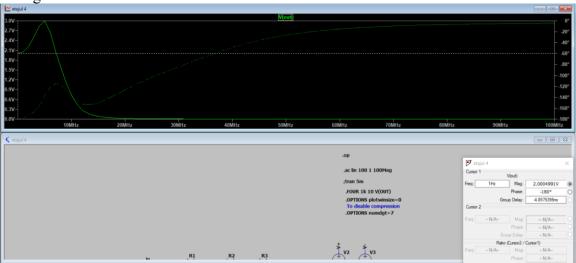



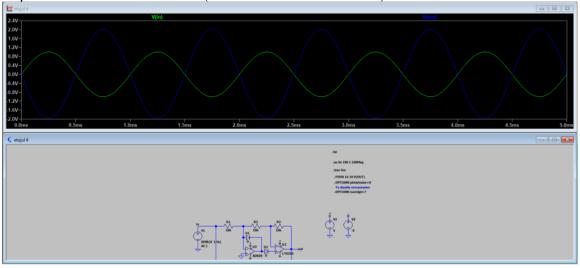

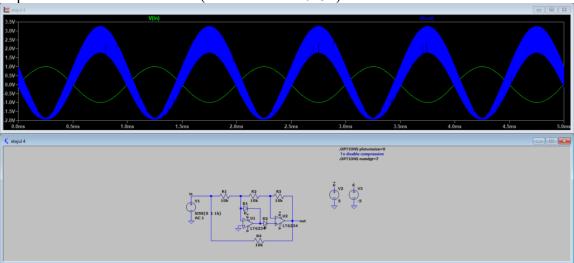Implementare functie de circuit(doar cu AO LT6234)



2. Concluzii

Compararea rezultatelor obtinute cu cerintele impuse:

Cerinte impuse:

Ι	Etaj 1				Etaj 2			Etaj 3				Etaj 4		AO						
	Sursa semnal	amplitudine minima (pt castig maxim PGA)	amplitudine maxima (pt castig minim PGA)	unitate masura	Tip Etaj 1	Castig etaj 1 (liniar)	tip Etaj 2	H0 castig liniar in banda de trecere	Rintrare minim	Banda	٥	tip Etaj 3	castig minim [dB]	rezolutie (pas minim) [dB]	nr pasi	castig maxim [dB]	Rintrare minim	tip Etaj 4	Castig etaj 4 (liniar)	Tip AO
- 1	4	2.00E-05		A (differential)	6	10000	9	1	2.00E+03	5.00E+03	1.41	5	12	2	5	20		6	2	4

Rezultate obtinute:

Etaj 1:

Castig(liniar):9.99Kv Banda etaj1:1.85MHz

Etaj 2:

Castig (liniar) in banda de trecere: 998.44mV

Banda:4.966kHz

Etajul 3:

Castig=12dB(cerinte):12dB masurat

Banda:14.33MHz

Castig=14dB(cerinte):14dB masurat

Banda: 12.29MHz:

Castig=16dB(cerinte):15.99dB masurat

Banda:10.61MHz:

Castig=18dB(cerinte):18.06dB masurat

Banda:9.065MHz

Castig=20dB(cerinte):20dB masurat

Banda:7.65MHz

Etaj 4:

Castig liniar=2(cerinte):2 masurat

